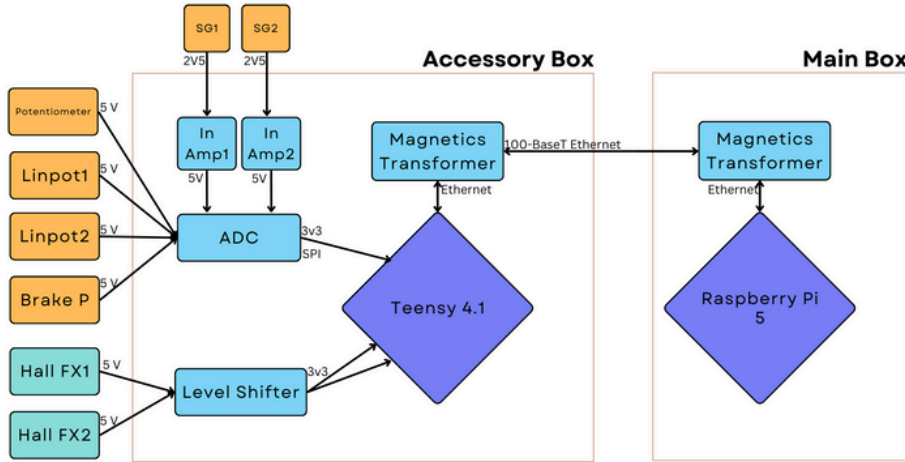


DATA ACQUISITION PCB FOR A/D SENSORS - BLUE JAY RACING

(Revision 1)


Signal Architecture



Purpose

- Design a circuit that reads the strain, speed, pressure, suspension, and distance traveled for an off-road vehicle
- Performed a **needs analysis** to initiate the design process

Key:

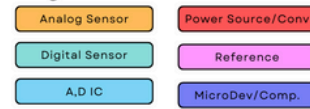

Revision 1:

- All sensors in black were implemented for the first revision

2 Accessory (DAQ) PCBs on car: 1) Front 2) Rear

Front	
Digital	Analog
5V FL axle Hall (9 mA max)	5V FL Linpot
FR axle Hall (9 mA max)	FR Linpot
Prop Shaft. Hall (20 kHz)	F Brake Pressure
FL Magnetometer (I2C, ~1 kHz)	2V5 FL Tie Rod SG (120 Ω , Q Bridge)
FR Magnetometer	FR Tie Rod SG
	5V Steering Potent.


Rear	
Digital	Analog
5V CVT Primary Hall (Tach) (9 mA max)	5V RL Linpot
Brake Rotor Hall (WS) (9 mA max)	RR Linpot
Rear Axle Hall (position) (9 mA max)	R Brake Pressure
RL Magnetometer (I2C)	
RR Magnetometer	

21XT Vehicle

Sensor Placement


General Sensors

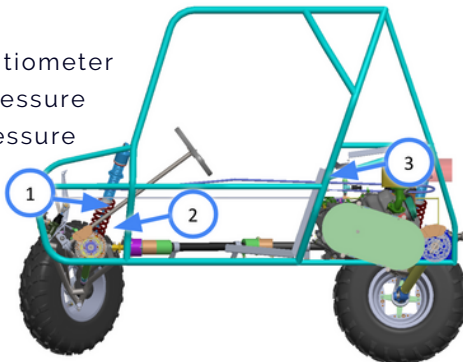- Steering Potentiometer
- Front Brake Pressure
- Rear Brake Pressure




Front Sensors

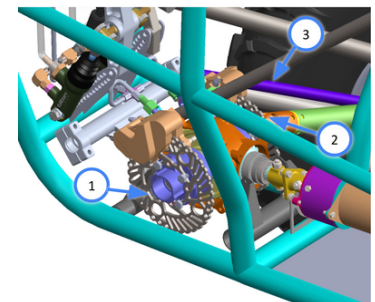- FL Axle Hall Effect
- FR Axle Hall Effect
- Tie Rod Strain Gauges (x2)




Rear Hall Effect Sensors

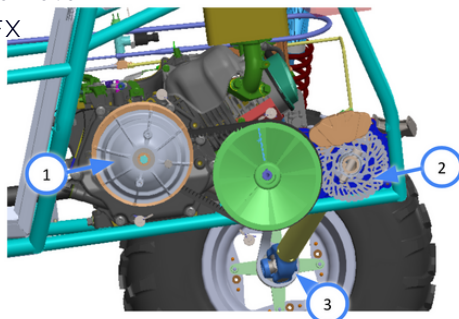- CVT Primary Tachometer
- Brake Rotor Hall FX
- Rear Axle Hall FX




Suspension Sensors

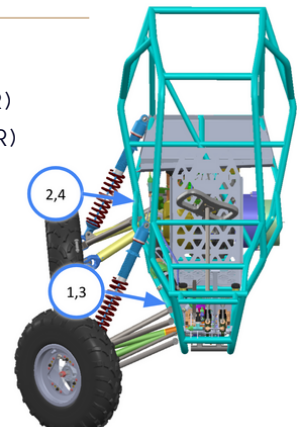- FL Magnetometer (x2 for FR)
- RL Magnetometer (x2 for RR)
- FL Linear Potentiometer (x2 for FR)
- RL Linear Potentiometer (x2 for FR)



DATA ACQUISITION PCB FOR A/D SENSORS - BLUE JAY RACING


Power Architecture

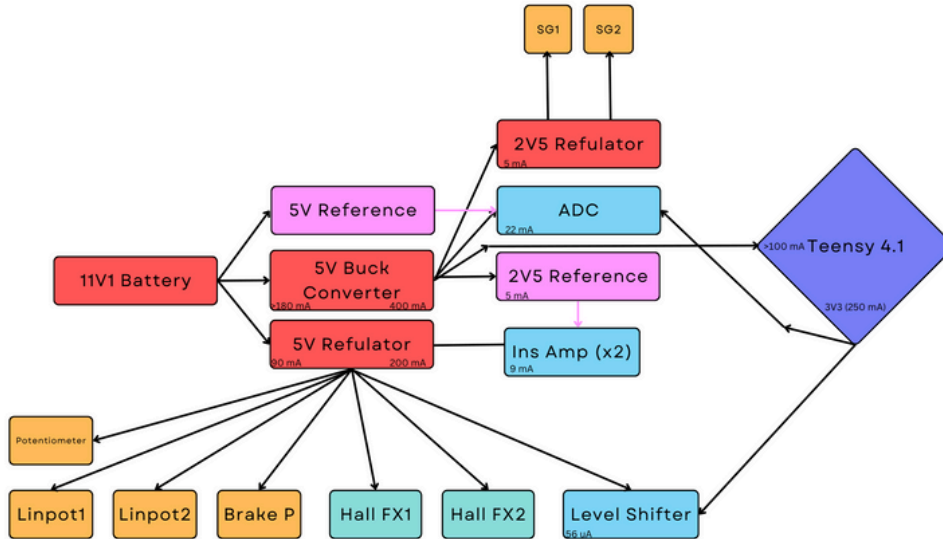


Requirements

- Design a system that is able to support 5V analog and digital sensors, and 2.5V differential analog sensors
- Verify the power sourcing and sinking capabilities of all ICs

Key:

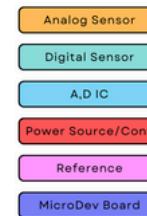

Schematic & PCB Design

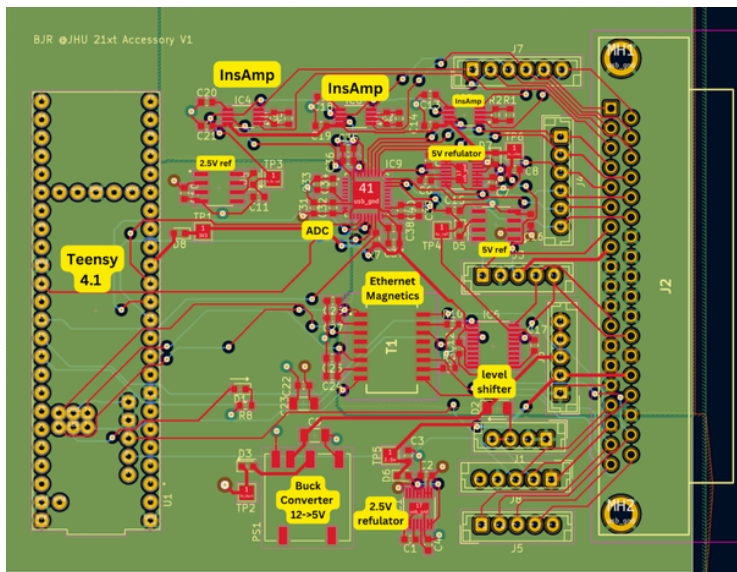

96.5 mm x 79 mm

Results

- Power ICs and ADC operated within expectations
- Ethernet successfully transmitted at 100 Mbps
- Increased sensor capacity by 33% from 20XT
- Teensy 4.1 was able to be programmed and successfully read

Design Process

- Used KiCAD to design schematic and PCB
- Implemented Teensy 4.1 Dev. Board for its strong CPU performance & RAM
- Selected DC37 Connector along with testing connectors

Testing Procedure

- Tested for power and ADC signal connectivity
- Confirm buck converter, reference, and regulator stability
- Measured ADC output SNR
- Analyzed Teensy 4.1 Program Output

